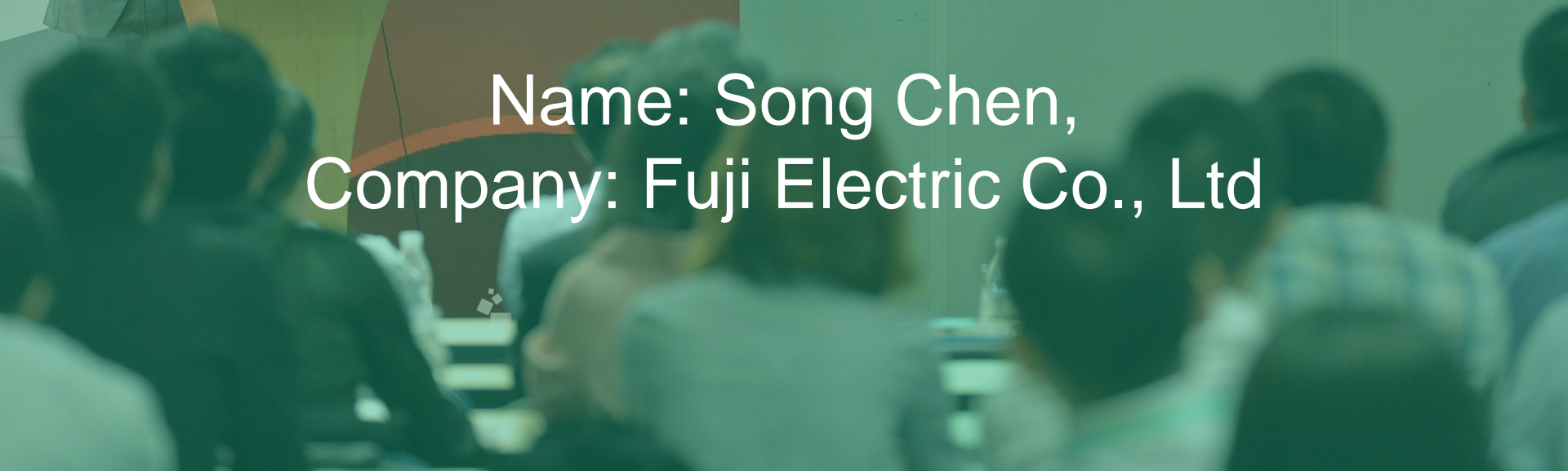


pcim
ASIA

North China Electrical Power University
 University National San Luis Gonzaga de Ica
 University of Chinese Academy of Science
 Xi'an Jiaotong University
 University

2.3kV Si and SiC devices development for renewable energy system

Name: Song Chen,
 Company: Fuji Electric Co., Ltd



- Introduction
- Technology of 2.3kV Si device
- Technology of 2.3kV SiC-MOSFET device
- Static characteristics: I-V curves of IGBT/MOSFET devices
- Static characteristics: I-V curves of FWD/MOSFET devices
- Switching waveforms of 2.3kV Si device
- Switching waveforms of 2.3kV SiC-MOSFET device
- Power dissipation comparison
- Conclusion



Motivation

DC-link voltage $\sim 1500\text{V}$ is required for renewable energy applications.

- ◆ 2-level topology with 3.3kV devices:
 - Large switching losses due to the high blocking voltage device.
- ◆ 3-level NPC topology with 1.2kV devices:
 - Large number of devices and gate drives
 - Bigger commutation inductance

Our Proposal

New 2.3kV devices for renewable energy systems.

- ◆ Advantages of 2-level topology with 2.3kV devices:
 - ✓ Smaller footprint size
 - ✓ Smaller number of gate drivers
 - ✓ Lower on-state losses
 - ✓ Lower commutation inductance




Technology of 2.3kV Si IGBT

- ◆ 2.3kV Si-IGBT device based on the 7th Gen technology
- ◆ Thinner drift layer
- ◆ Low on-state voltage and low conduction loss

Cross section view of Si-IGBT chip

Technologies of 7G IGBT

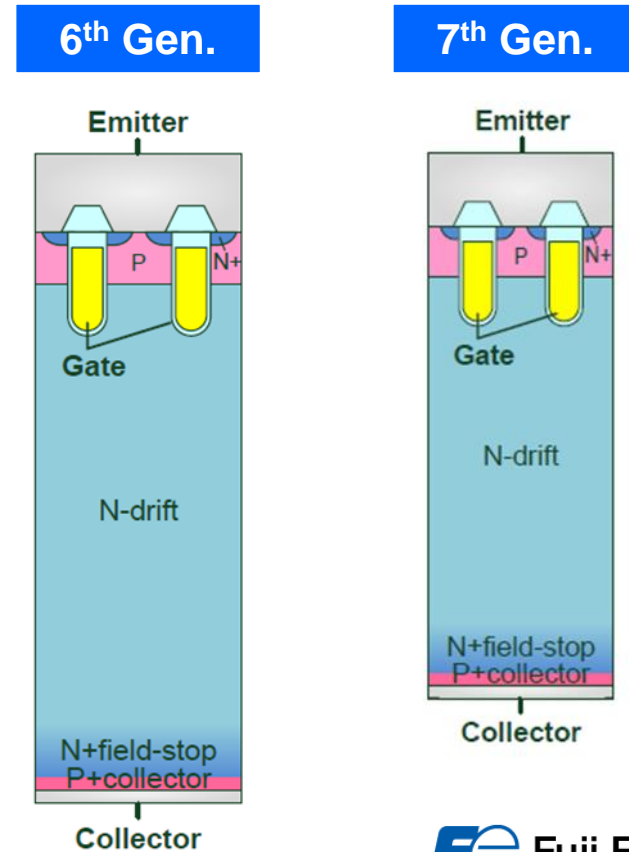- Thinner drift layer
 - Reduce $V_{CE(sat)}$ and E_{off}
- More fine pattern of trench pitch
 - Reduce $V_{CE(sat)}$ and E_{off}
- Optimized Field-Stop layer
 - Secure breakdown voltage
 - Low leakage current at high temperature




Technology of 2.3kV SiC-MOSFET

Fuji 2nd Gen SiC-MOSFET has 23% lower R_{on} than Fuji 1st Gen SiC-MOSFET by shrinking the cell pitch.

Technologies of Low R_{on}



- Narrow cell pitch
- Thin N+ substrate
- Trench gate structure

Cross section view of SiC-MOSFET

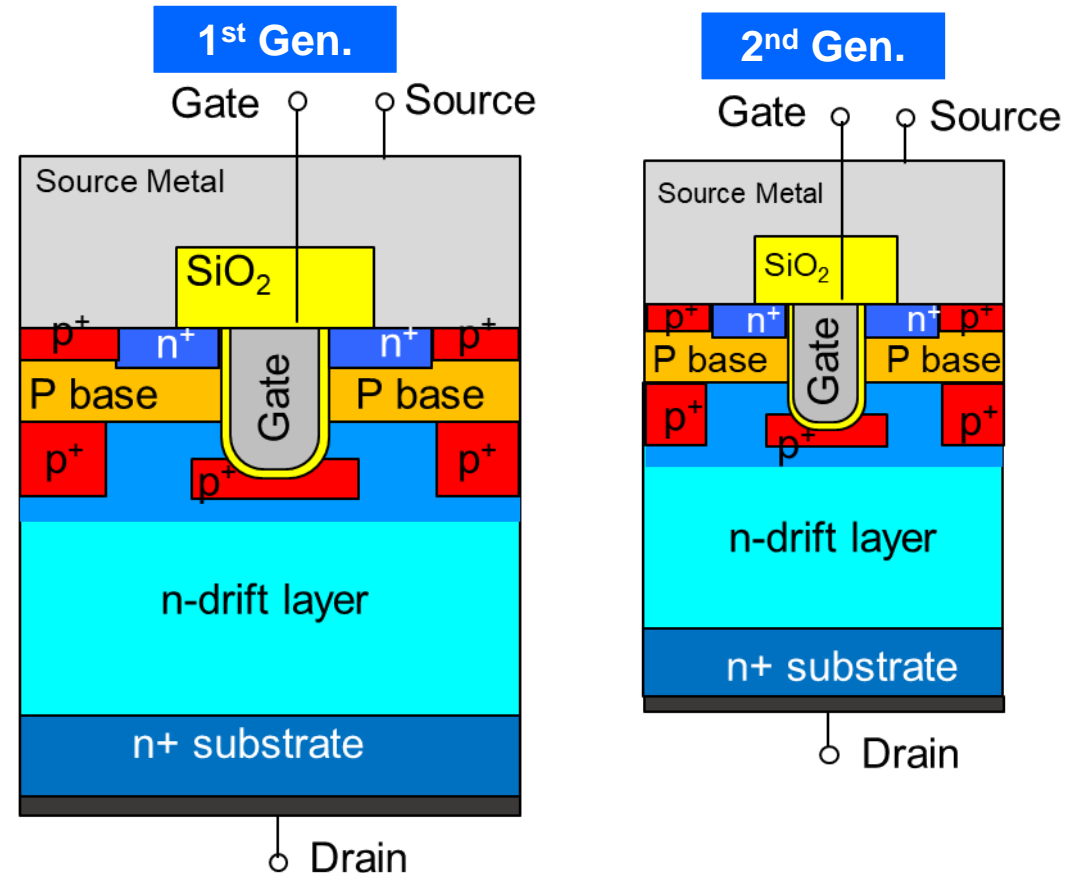



Compared to 1.2kV Si IGBT in 3-level NPC circuit,

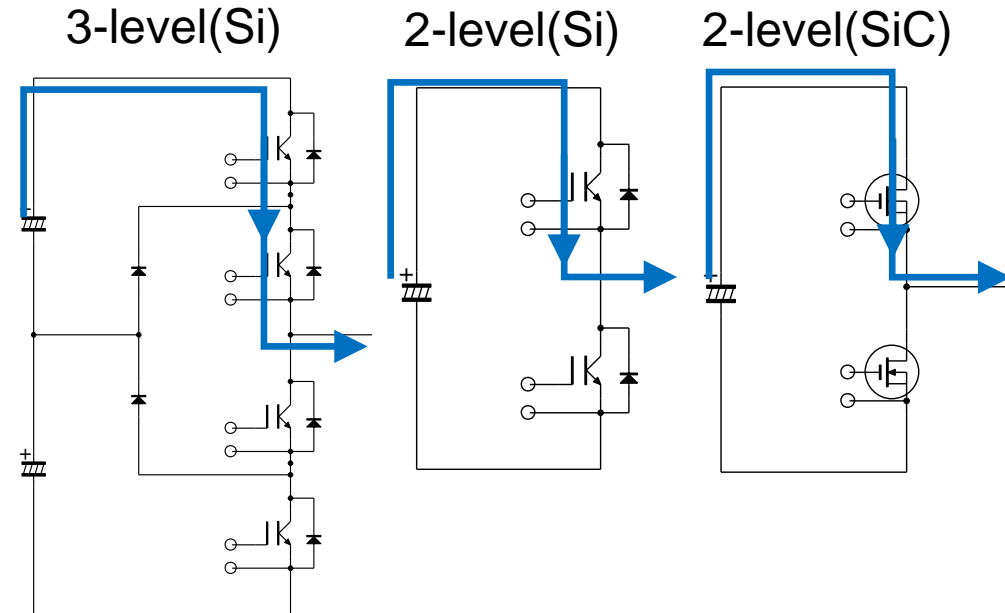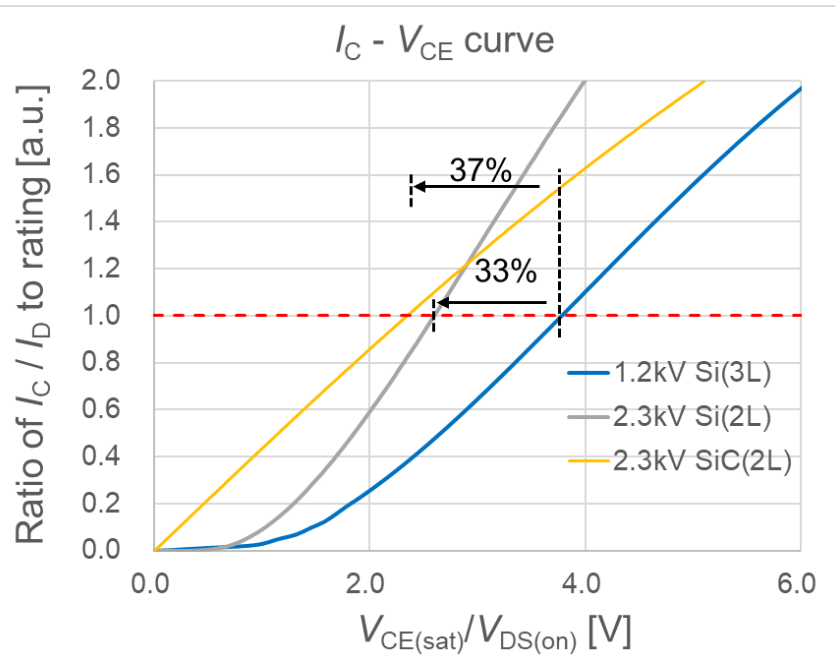- ◆ 2.3kV Si IGBT in 2-level circuit is 33% smaller.
- ◆ 2.3kV SiC-MOSFET in 2-level circuit is 37% smaller.



Compared to 1.2kV Si FWD in 3-level NPC circuit,

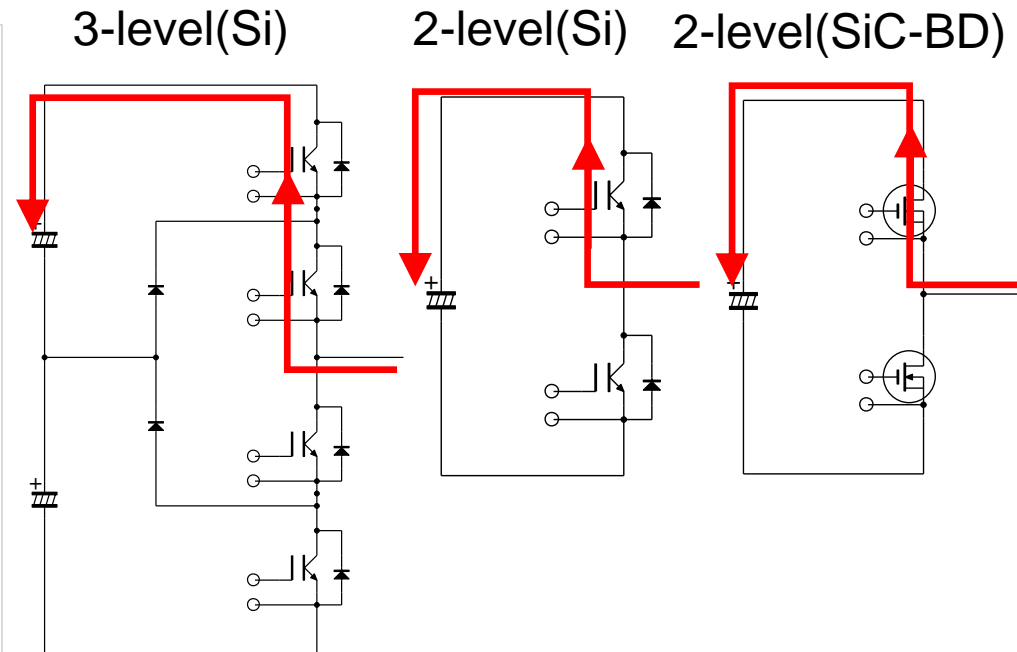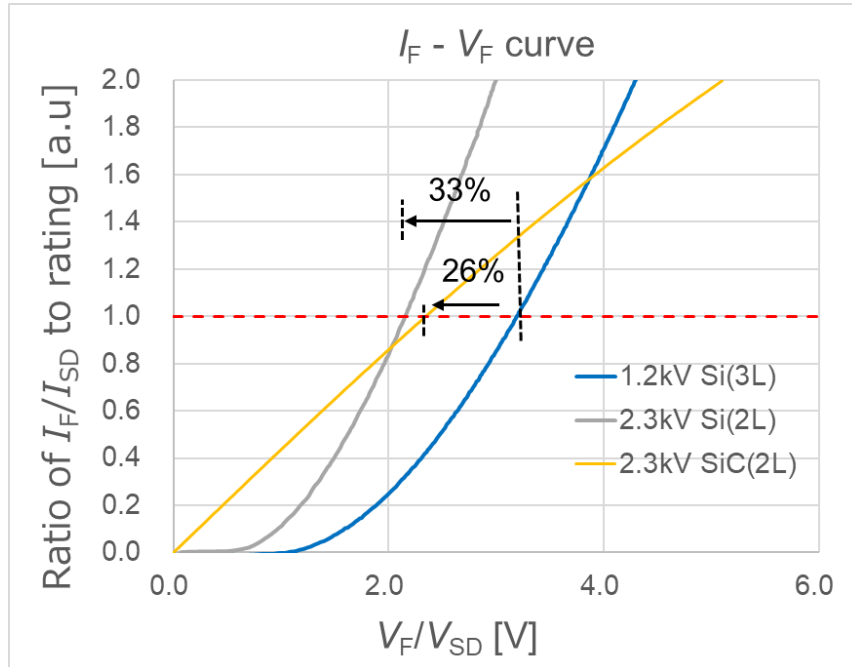
- ◆ 2.3kV Si FWD in 2-level circuit is 33% smaller.
- ◆ 2.3kV SiC-MOSFET (Body Diode) in 2-level circuit is 26% smaller.




Switching Waveforms of 2.3kV Si-IGBT

- ◆ Larger turn-off and reverse recovery tail current at higher temperature
- ◆ Smaller di/dt at higher temperature
- ◆ Larger switching losses at the higher temperature


Turn-on waveform

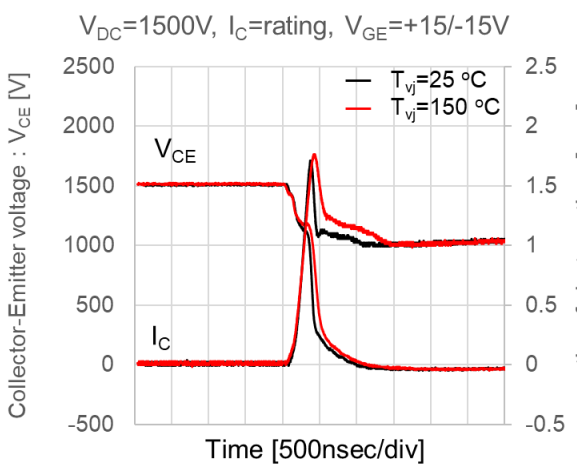

Turn-off waveform

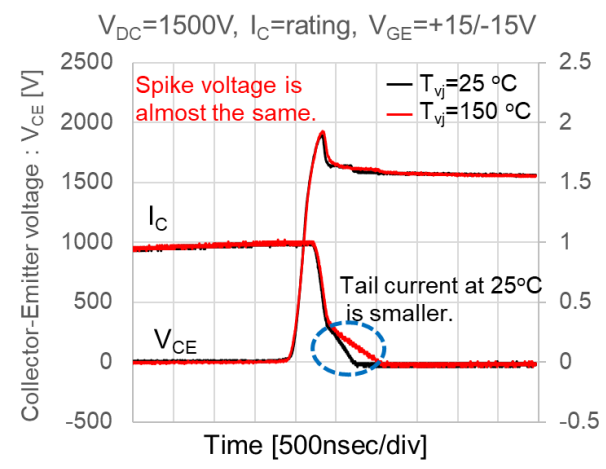

Reverse recovery waveform

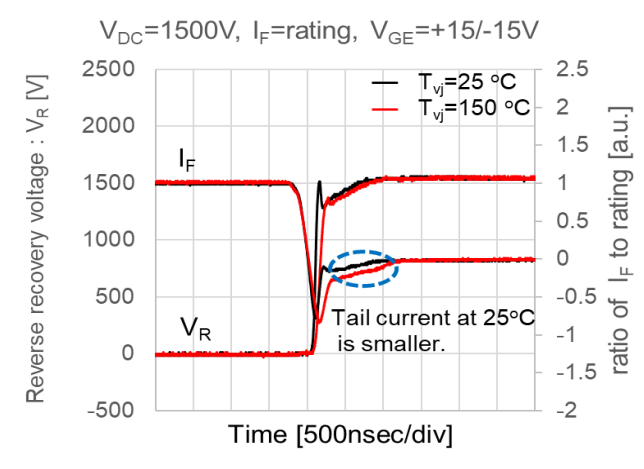


Switching Waveforms of 2.3kV SiC-MOSFET


pcim
ASIA

- ◆ No tail current and small spike
- ◆ Smaller spike voltage at higher temperature


Turn-on waveform

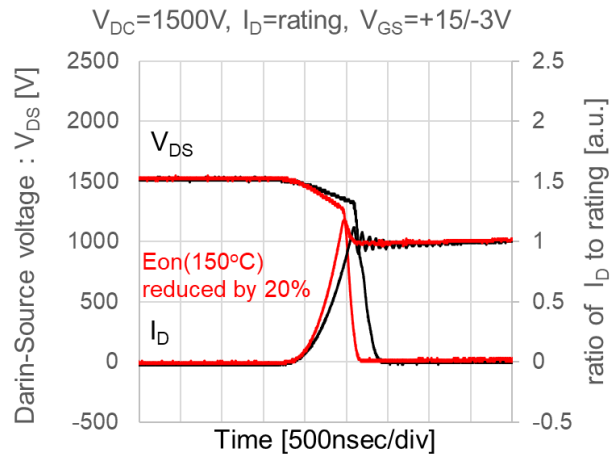

Turn-off waveform

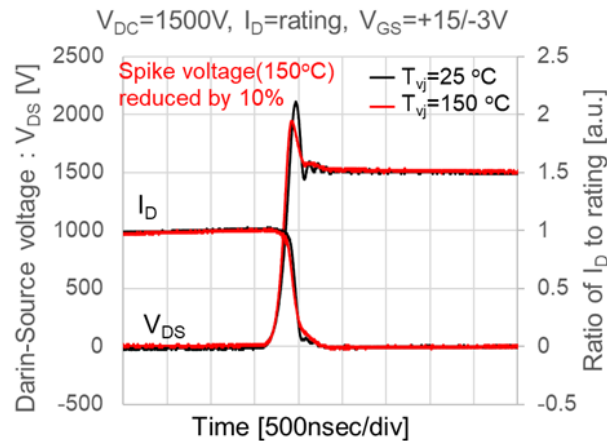


Reverse recovery waveform

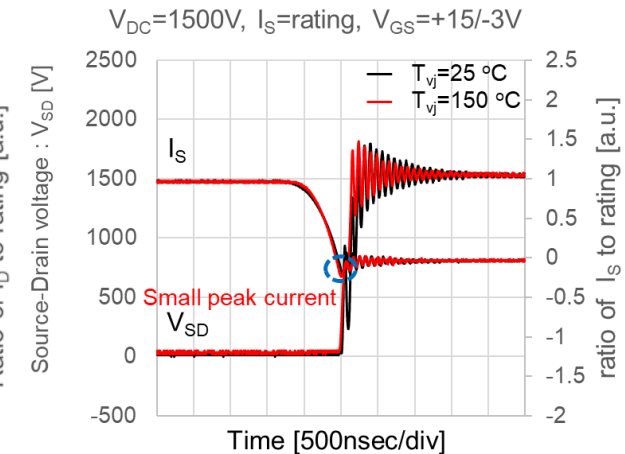

Power Dissipation Comparison


Conditions of $I_o=600\text{Arms}$, $V_{DC}=1500\text{V}$, $\cos\phi=1$, $\lambda=1.0$, $f_c=1\text{ kHz}$, $T_{vj}=150\text{ degC}$.

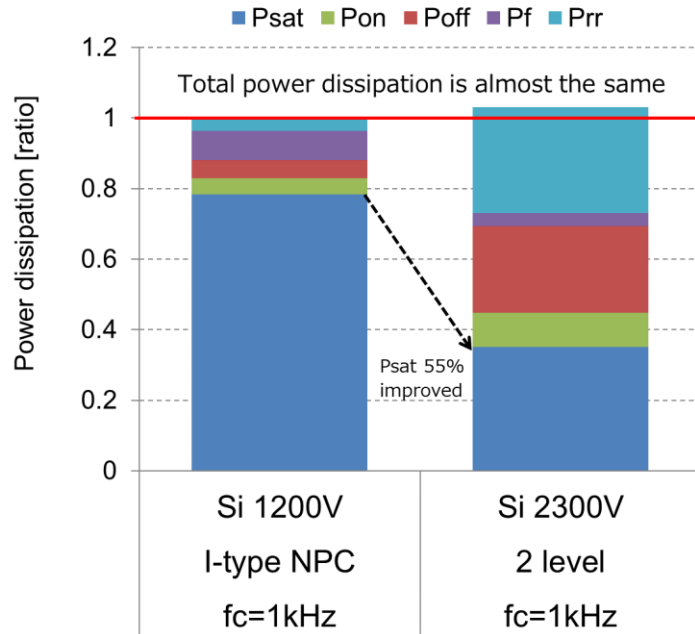2-level topology with 2.3kV Si IGBT and
3-level NPC topology with 1.2kV Si IGBT



The total power dissipation is almost the same.

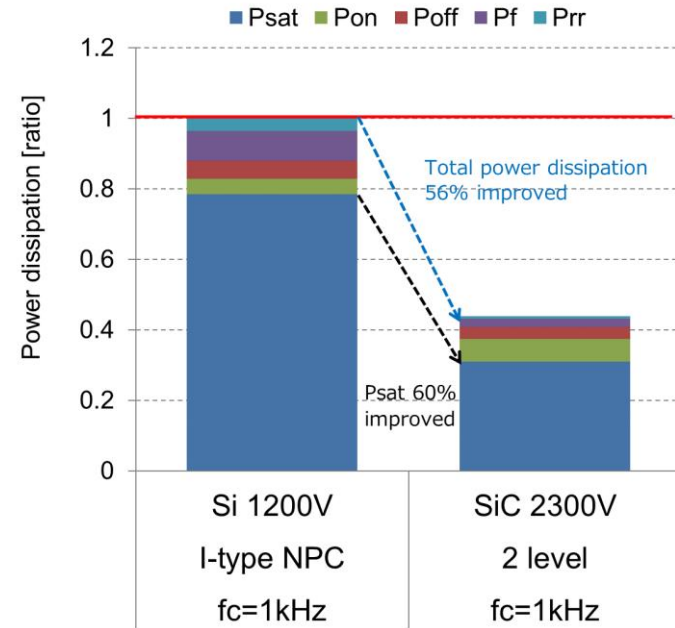2-level topology with 2.3kV SiC MOSFET and
3-level NPC topology with 1.2kV Si IGBT



SiC device has better performance.

Benefits of 2.3kV device in 2-level topology

✓ Simplified circuits and drives, reduced dissipation losses

	3-level (Si)	2-level (Si)	2-level (SiC)
Number of devices	30 😞 (IGBT x12, FWD x18)	12 😞 (IGBT x6, FWDx6)	6 😊 (MOSFET x6)
Footprint	100% 😞	33% 😊	33% 😊
Number of gate drivers	12 😞	6 😊	6 😊
Total loss	100% 😞	103% 😞	44% 😊
On-state loss	100% 😞	45% 😊	38% 😊
Switching loss	100% 😞	487% 😞	80% 😊

- Newly developed 2.3kV Si-IGBT and 2.3kV SiC-MOSFET with trench gate structure have been introduced.
- The 2.3kV devices are suitable for renewable energy applications with ~1500VDC bus voltage.
- The 2.3kV SiC-MOSFET has low power dissipation, and it can operate at higher switching frequency.
- The 2.3kV devices have the following benefits:
 - Simplified inverter design with a small number of gate drives
 - Low commutation inductance
 - Low on-state loss